

ELECTRICAL ENGINEERING DEPARTMENT  
EEL101 PRINCIPLES OF ELECTRICAL ENGINEERING  
MAJOR TEST

Date: November 21, 2008

Time: 3:30PM to 5:30PM

Q1. In the circuit of Fig. Q1, find the current  $I_c$  as a function of time for  $t > 0$ . The switch  $S_1$  is closed at time  $t=0$  while switch  $S_2$  is opened at time  $t = 0.0$ . Before being opened switch  $S_2$  was closed for a long time.

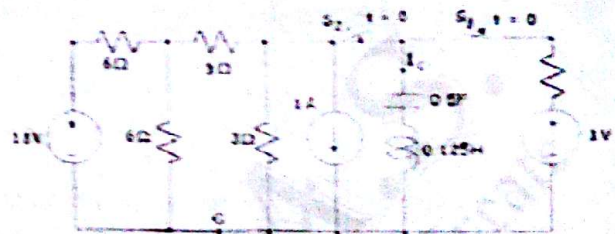


Fig. Q1

$I_c = (\frac{1}{s} - \frac{1}{s})$

Q2. For the op-amp circuit in Fig Q2, find the output voltage  $V_{out}/V_{in}$ .

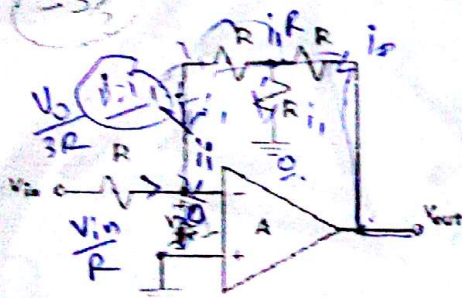


Fig. Q2

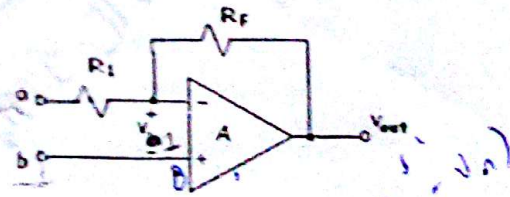


Fig. Q3

Q3. In the op-amp circuit shown in Fig Q2,  $A=5 \times 10^5$ ,  $R_1=1 \Omega$ ,  $R_f=100 \Omega$ ,  $V_1=50 \mu V$ .

- (i) What is the output voltage  $V_{out}$ ?  $-25$
- (ii) Which of the terminals a or b ought to be grounded and which given the input?
- (iii) What is the input voltage to be applied.  $25 \text{ Volts}$

Q4. A magnetic circuit comprises of three parts in series, each of uniform cross sectional area. They are,

1. A length of 80 mm and cross sectional area  $50 \text{ mm}^2$
2. A length of 60 mm and cross sectional area  $90 \text{ mm}^2$
3. An air gap of length of 0.5 mm and cross sectional area  $150 \text{ mm}^2$

Assuming that all flux flow through the given circuit and the  $\mu_r$  of the magnetic material is 1200, estimate the current required to produce a flux density of 0.3T across the air gap. The coil of 4000 turns is wound on the leg with cross sectional area  $90 \text{ mm}^2$ .

$0.46 \text{ amperes}$

