

DEPARTMENT OF ELECTRICAL ENGINEERING IIT DELHI

EEL101 FUNDAMENTALS OF ELECTRICAL ENGINEERING

Max. Marks 35

Major Test II (19/11/2011)

Time 120 min.

(a) Attempt ALL questions. (b) Open Class notes Test.

Q1. Find node voltages for the circuit shown in Fig.1. Given $V_s=20$ V. (4)

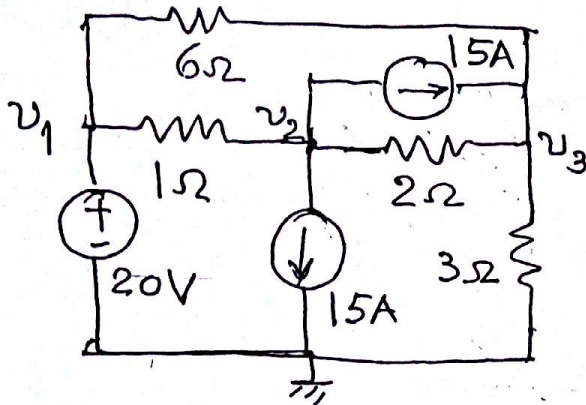


Fig. 1

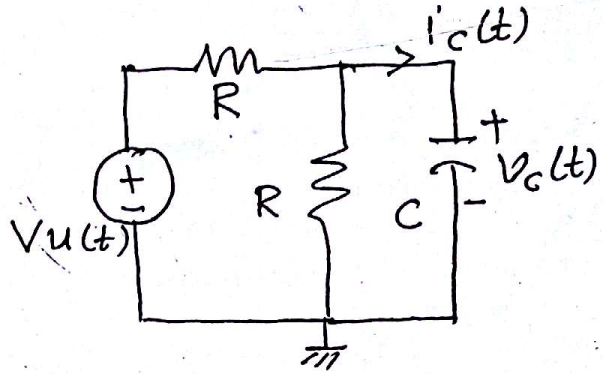


Fig 2

Q2. For the circuit in Fig. 2 find the step responses for capacitor current $i_c(t)$ and voltage $v_c(t)$. Sketch $i_c(t)$ and $v_c(t)$. (4)

Q3. Calculate resonance frequency of the admittance circuit shown in Fig.3. When a voltage source $v_s(t) = \cos 3t$ is applied to the admittance circuit, find: (a) Energy stored in the inductor $W_L(t)$, (b) Energy stored in the capacitor $W_C(t)$ and (c) Maximum total energy stored W_{max} . (5)

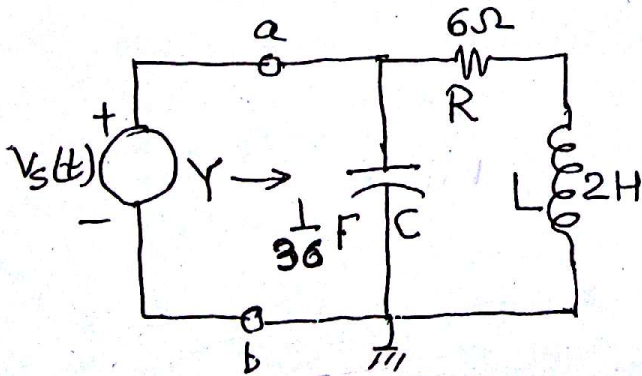


Fig. 3


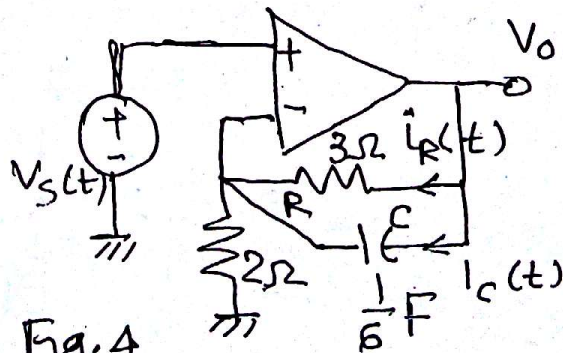


Fig. 4

Q4. For the op-amp circuit shown in Fig.4 find: (a) $v_o(t)$, (b) $i_R(t)$ and $i_c(t)$ when $v_s(t) = 6 \sin 3t u(t)$. (4)

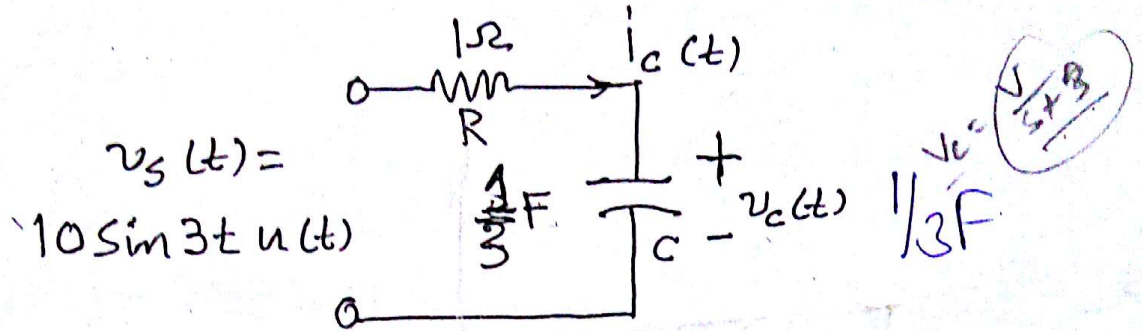Q5. Applying Laplace Transform determine the response $i_c(t)$ and $v_c(t)$ to a sinusoidal excitation $v_s(t) = 10\sin 3t u(t)$ for the circuit shown in Fig.5. (4)



Q6. For a 2400:240V, 50Hz, 48kVA 1-phase transformer open and short circuit tests conducted with low voltage winding as primary, show the following readings: $W_{OC} = 380$ W, $I_{OC} = 3.8$ A, $W_{SC} = 400$ W and $V_{SC} = 4.5$ V. Calculate the transformer core loss resistance R_C , magnetizing reactance X_M , net series resistance R_{SC} and leakage reactance X_{SC} from low voltage end. Draw corresponding equivalent circuit. What will be the values of these parameters if the tests were conducted from the high voltage end? (4)

Q7. A DC shunt motor has 12 kW rated input power at 100V rated input voltage when it runs at rated speed of 1000rpm. It draws 6A current at no load. Motor armature resistance is 0.1Ω . Calculate (a) Rated input current, (b) Rated electromagnetic torque produced by the motor, (c) no load speed and (d) Speed regulation when rated load is withdrawn from the motor. Neglect friction torque. (4)

Q8 (a). Using graphical method, explain production of rotating field in a basic 3-phase, 2-pole, 6-slot cylindrical rotor AC synchronous generator, due to balanced 3-phase currents $i_A = I_M \cos 314t$ A, $i_B = I_M \cos(314t - 2\pi/3)$ A and $i_C = I_M \cos(314t - 4\pi/3)$ A flowing in its armature winding, by showing the resultant field at $t = 0$ s, 1.666 ms and 3.33ms. (3)

(b) A 3-phase Y-connected AC synchronous generator has rated phase voltage of 150V for a rated load at 0.8 power factor lagging. Find the synchronous reactance of the generator X_S when the generated induced voltage E_F is 219V. Also calculate the torque angle δ_G . Draw corresponding phasor diagram. Neglect the armature resistance. 10 kVA (3)

